

RELEVANT PRODUCTS

- AWT6223

INTRODUCTION

This WEDGE Power Amplifier Module supports GSM type dual, tri and quad band applications for GMSK and 8-PSK modulation schemes using a polar architecture, as well as WCDMA in the IMT band. The WEDGE module includes an internal reference voltage and integrated power control scheme for use in GMSK and 8-PSK operation, which facilitates fast and easy production calibration and reduces the number of external components required to complete a power control function. This integrated control loop reduces the development time associated with optimizing loop filters to meet time mask and switching transient requirements, as it is completely self-contained.


The module size is a competitive 6 mm x 8 mm and with the few external components required, it is well suited for a small form factor transmit front-end solution.

GENERAL DESCRIPTION

The application circuit below shows the relative ease with which this amplifier can be designed into a GSM transmit front-end. All of the RF ports for this device are internally matched to 50Ω.

The RF inputs can interface to transmit VCO's with the addition of simple attenuators. These can be used to set the input drive to the PA and is generally good practice to help minimize any possible load pulling effects at the VCO, PA interface. The RF outputs can interface directly to an antenna switch module to complete the front-end solution.

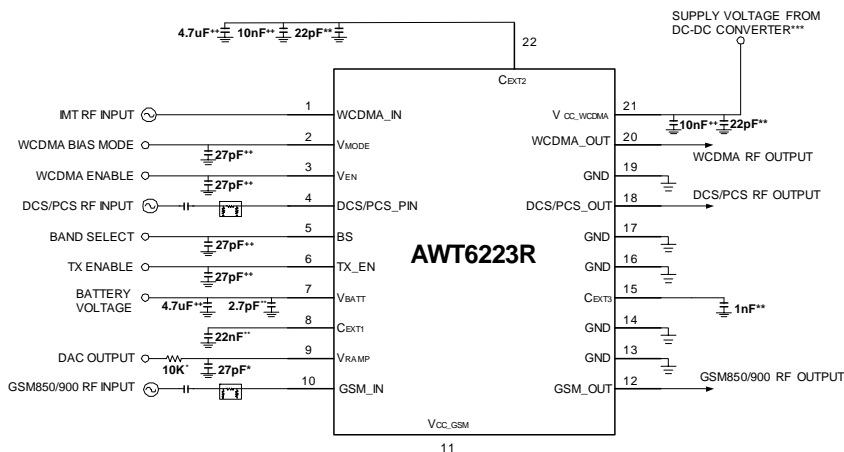The logical control inputs, TX_EN and BS, are both 1.8 V and 3 V logic compliant. The TX_EN is used to enable the amplifier typically with the TX burst. The BS is used to select which amplifier is enabled.



* Filtering may be required to filter noise from baseband.

** This component should be placed as close to the device pin as possible.

*** If the final design uses a DC-DC Converter, otherwise connect Pin 21 directly to V_{BATT}.

++ These components are recommended as good design practice for improving noise rejection characteristics. The values specified are not critical as they may not be required in the final application.

Figure 1: Recommended Application Circuit

POWER CONTROL

The scheme used is a closed loop method that requires only the application of an analog voltage to the VRAMP pin to set the output power. This can be applied directly from a standard DAC output. The method used does not require any power or current sensing. Setting the VRAMP voltage, in turn sets the collector voltages of the power amplifiers to a multiple of the VRAMP voltage using a pre-determined formula. This collector voltage is regulated in a voltage control loop as shown below. The amplifier's bias is held constant while the collector voltage is adjusted to set the power. The relationship between the output power and collector voltage is described by Equation 1.

$$P_{OUT} (Watts) = \frac{(2 \cdot V_{CC} - V_{SAT})^2}{8 \cdot R_{LOAD}}$$

Equation 1

where VCC, VSAT are the collector voltage and saturation voltage of the transistor respectively. This

expression shows how the power variation due to VBATT is limited due to voltage control loop.

Under extreme conditions, as the battery voltage degrades, it is important to maintain the control loop bandwidth, so the collector voltage quickly follows VRAMP. This is done by adjusting VRAMP, such that:

$$V_{RAMP} \leq 0.38 \cdot V_{BATT} + 0.20 \leq 1.6V$$

Equation 2

The effect of the loop bandwidth slowing can be seen most clearly in the switching transients measurement. This adjustment can be incorporated in the software of the final application, so that performance is enhanced under low voltage conditions. Another advantage of this control scheme is the improved noise performance due to individual stages being held in compression, thus improving the overall receive band noise performance.

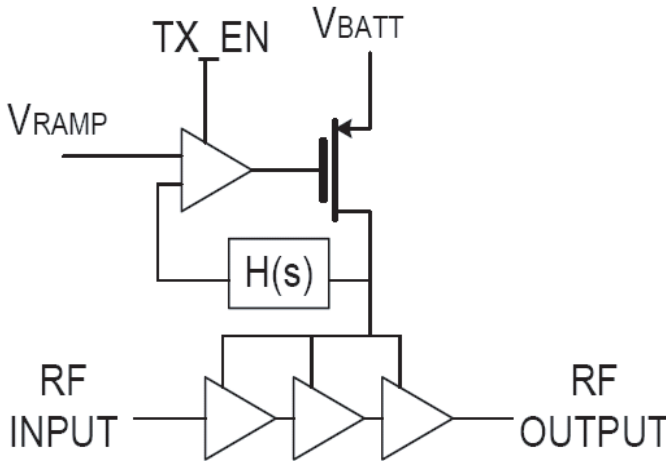


Figure 2: Voltage Control Loop

DESIGN RECOMMENDATIONS

1. RF DECOUPLING

To comply with any potential radiated contribution around the PAM mostly related to PCB design it is good practice to place two RF decoupling ceramic capacitors on pins 7 and 22 of the AWT6223, as close to the PAM as possible. Also, provision should be made to bypass V_{BATT} at the battery connector with the same level of decoupling. This can be accomplished by placing two ceramic capacitors similar to the one at V_{BATT} pin 7 as close as possible to the V_{BATT} pin of the battery connector. The grounding of any bypass capacitors is critical to achieve the expected improvements. All GND for decoupling capacitors should be connected to the main GND-plane as directly as possible preferably using microvias, see PCB cutout in Figure 3.

 


Figure 3: Example of GND Connection from Pad Using Microvia and Buried Via

The values of the capacitors chosen depend on their location, grounding and physical size. These factors determine the resonant frequency at which the decoupling is most effective. One cap should be optimized for the GSM850/900 band performance, the other for DCS/PCS and IMT. The V_{BATT} line to the AWT6223 pin 7 should be kept as short as possible and preferably shielded inside the PCB between two GND layers (known as stripline) in order to suppress radiation originating from this line.

2. INPUT POWER

The GSM quad-band part of the AWT6223 operates over the 0 to 5 dBm range and has been optimized for best typical performance at 3 dBm. ANADIGICS recommends a series capacitor and resistive

attenuator to be placed between the VCO and PAM. Some transceiver designs require a capacitor between the VCO output of the chipset and the resistive attenuator on the input of the PAM because the VCO output has a DC offset. The attenuator helps prevent load pulling of the VCO by further improving the return loss and also gives the flexibility to optimize the input drive to the PAM, which will depend on the transceiver output power and losses prior to the PAM. In order to avoid potential problems of strong RF signals radiating or coupling to other parts of the circuit, we suggest that the attenuator is placed as close to the transceiver chip VCO output as possible.

3. MATCHING BETWEEN PA AND ANTENNA SWITCH MODULE (ASM)

Provision should be made for matching the ASM to 50 ohms. Though the ASM usually specifies 50 ohms impedance, the actual impedance on the PCB is dependent on the transmission lines at the PA interface, and any vias and buried layer routing. This is rarely 50 ohms. A T-network or π -network is recommended for the matching as this gives sufficient flexibility. The component values used for the matching are dependent on the impedance presented by the ASM used.

4. ANALOG RAMP VOLTAGE INPUT

At the GSM/EDGE V_{RAMP} input pin 9 an analog voltage to set the output power can be applied directly from a standard DAC output. In order to smooth this DAC output staircase shaped signal, it is recommended to make provision for an RC filter. The values for this filtering depend on DAC bit resolution and sample rate.

5. WCDMA PA OUTPUT

The majority of current WCDMA design solutions using ANADIGICS WCDMA PAMs do not require an isolator or circulator in the front end design in order to reject any reverse signal from the duplex filter and antenna due to mismatch. The impedance of the duplex filter often changes in the upper TX frequency area where it is about to cut off and filter out TX signals in order to separate TX & RX as the upper TX frequency is closest to the RX frequency area. The load deviates from the ideal 50 Ω and increases the mismatch seen at the WCDMA PA output. The WCDMA PA stage would in most cases be able to address this, by decreasing output power by a relative small level of approximately 1 dB.

6. PCB LAYOUT GROUNDING

To have the best performance good grounding is crucial. "Local ground planes" only connected to the board GND plane using a few microvias is not adequate. All GND planes must be connected to the main GND layer (one designated inner layer of the PCB) using a lot of through vias. Besides being the reference for the all RF and other signals, the GND plane is also used to distribute the heat dissipated by the PA and should therefore be sufficient size and with many through vias to spread the heat to other copper layers. In order to establish a good ground connection for the PA, it is necessary to assign an area on the first inner layer to GND. Microvias will go from the large GND pad under the PA to area on the first inner layer and buried or through vias will go the rest of the way to the ground plane in the center of the board, see Figure 4.

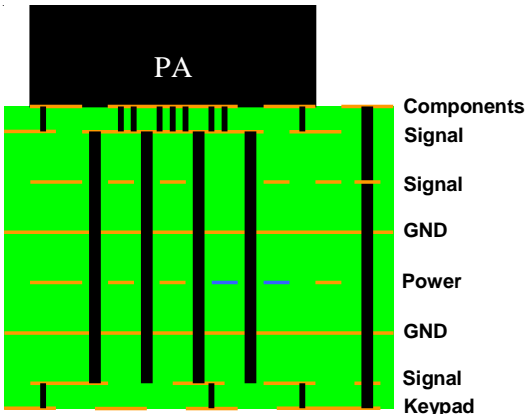


Figure 4: Example of PCB Stack-up with Microvias from Top and Bottom Layers, Buried Vias from Layers 2 to 7, and through Vias from Layers 1 to 8

For more information regarding GND underneath the PAM, please refer to the "Package Outline" chapter and the "Soldering Guidelines for Module PCB Mounting - Application Note". Generally, it is good practice to establish shielding around the PAM. For the shielding to be effective, a good GND-connection is also required. Therefore a lot of vias

should be used, where the shielding - whether it is metallized plastic or a traditional shielding can - is attached to the PCB surface, see Figure 5.

 


Figure 5: Example of Via Placement at Shielding Landpattern Close to PA

7. RF TRACKS

Keep RF tracks as short as possible and with as few corners and bends as possible. Make openings in the ground plane on the layer just under all 50 Ω pads on the PAM and the FEM (Front End Module) or ASM (Antenna Switch Module). The short distance between the component layer and the first inner layer is very small compared to the pad size. This means that the pads terminate the transmission line in low impedance much different from that of the track. The result of this is mismatch, which again can result in up to a couple of dB loss of signal. As a rule, ANADIGICS normally uses a clearance around microstrips and striplines of at least the same width as that of the track, i.e. if the track width is 12 mil or 0.3 mm, the clearance on both sides of the track to any copper area is also 12 mil or 0.3 mm.

Generally, keep reference clock signals, digital signals or analog I and Q signals away from RF tracks and V_{BATT} connections. Make sure that these different signal connections are not running directly underneath or above RF tracks or V_{BATT}.

SETUP RECOMMENDATIONS

1. TIMING

In order to meet the ETSI specified GSM power time template and switching transients, the sequence of events outlined in Figure 6 is recommended. The timing on BS is not critical; it just needs to be enabled and settled prior to TX_EN going high (approx. 2 μ s). The PA “forward isolation 1” parameter and the

ASM isolation is met outside burst. The PA “forward isolation 2” parameter ensures the time template is met during the burst with sufficient margin. The timing of the TX_EN is critical to ensure the application has sufficient margin for meeting the burst timing requirement.

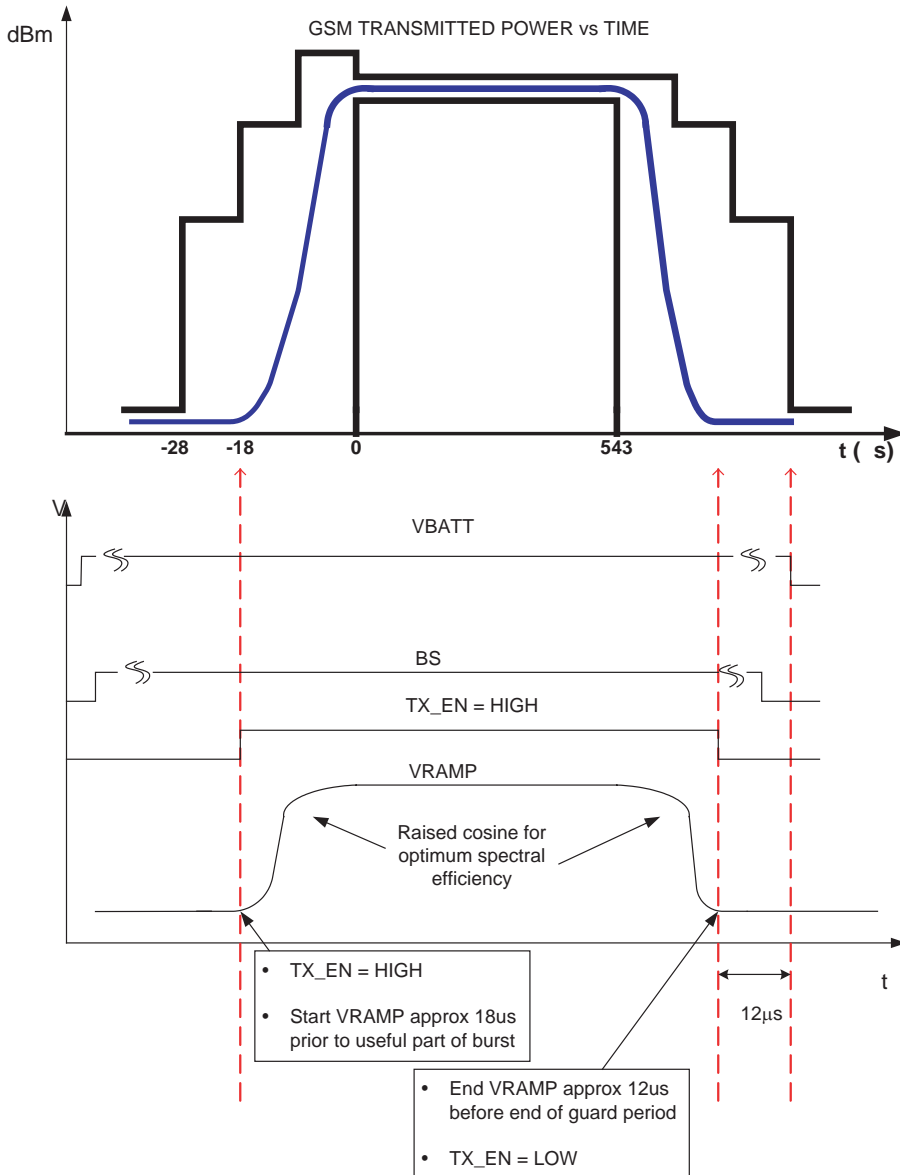


Figure 6: Timing Recommendations

WCDMA/GSM/GPRS/Polar EDGE Power Amplifier Module

The change in the power ramping profile could possible conflict with the timing of the PA. Since the signals like TX_EN are usually used to improve the isolation, it can be quite close to the V_{RAMP} ramping signal. If one of the control signals for instance controlling the ASM conflicts with the V_{RAMP} signal, it usually results in a very poor switching spectrum performance. In order to verify this, all the control signals for ASM, TX_EN, BS, etc. should be compared with the V_{RAMP} profile using an oscilloscope. The timing can affect the switching spectrum and the isolation. In Figure 7 and Figure 8 the yellow line [1] is the V_{RAMP} signal and the blue line [2] is TX_EN and the figures shows an example of how logic signals should be kept clear of the power ramping signal V_{RAMP} .

ramping with regard to switching spectrum when developing a new platform. This is usually not a complicated task, and can be done manually in a few hours. The power ramping affects switching spectrum, and have to meet the Power Time Template specified by ETSI. Generally, the ramp profile should be as close as possible to a raised cosine waveform. In Figures 9 and 10 is an example of a smooth shaped power ramping profile resulting in good switching spectrum performance, see Figure 11. The example is based on measurement results from a radio demo platform based on an ANADIGICS PAM and a standard transceiver. ANADIGICS baseband emulator provides the baseband signals for this platform.

2. POWER RAMPING

Since different PAMs have different control characteristics, it is necessary to optimize the power

 


Figure 7: Close in of the Timing With a Proper Distance Between the Logic TX_EN Signal and the Analog Power Ramping Signal V_{RAMP}

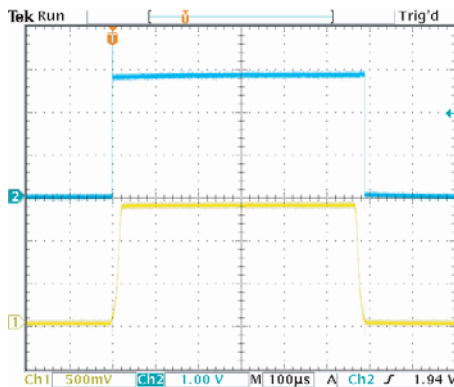


Figure 8: Total Timing Period of TX_EN & V_{RAMP} With a Proper Distance Between the Logic TX_EN Signal and the Analog Power Ramping Signal V_{RAMP}

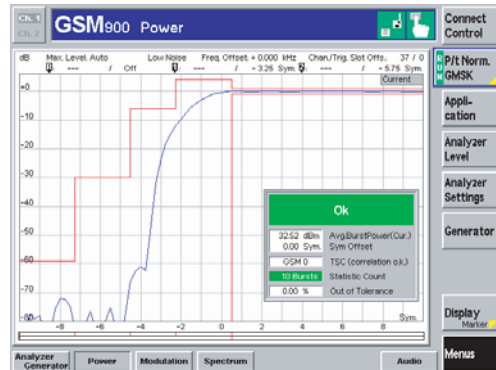


Figure 9: Rising Edge of a Smooth Power Ramping Profile Example Resulting in Good Switching Spectrum

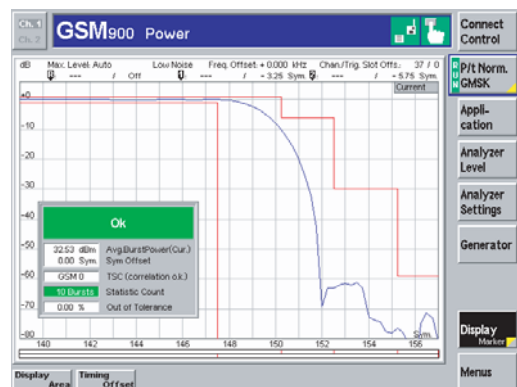


Figure 10: Falling Edge of a Smooth Power Ramping Profile Example Resulting in Good Switching Spectrum

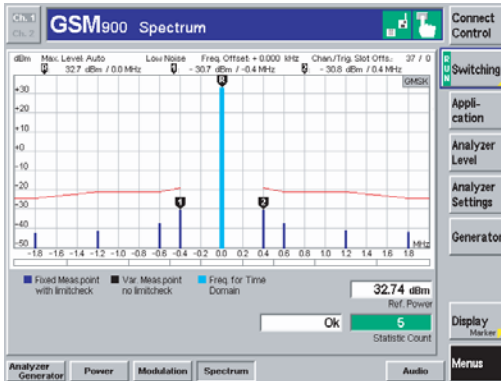


Figure 11: Corresponding Switching Spectrum Result from the Total Power Ramping Profile Shown in Figures 9 and 10

3. OUTPUT MATCHING OF THE PAM

Different PAMs will have different load contours. This means that they, in order to function at optimum performance, need to have the output matching circuitry tuned. The way to do this is by using the load contours provided by ANADIGICS and a network analyzer and then tune the matching network on the PA output toward the desired performance. The optimum matching network will usually be a compromise between output power, current consumption, and conducted harmonics. In most cases, $50\ \Omega$ is the best choice. In extreme cases, the switching spectrum can be affected if a poor matching solution is selected. This case is caused by the poor matching solution resulting in limiting the output power to the point of conflict with the ETSI specifications and forces the PAM close to saturation.

WCDMA MODE RECOMMENDATION

In order to maximize performance the ANADIGICS HELP™ WCDMA Bias Control functionality should be used, which enables the WCDMA PA to operate in Low and High Bias Modes thereby optimizing current consumption. Applying a logic level at V_{EN} pin 3 or V_{MODE} pin 2 corresponding to the desired PA Bias control mode controls this feature. Operation in the High Bias Mode allows the PA to exceed the system performance requirements at output power levels from +16 dBm to +28.5 dBm. For an output power less than +16 dBm, the Low Bias Mode should be used to minimize quiescent current while maintaining system performance. Setting the V_{EN} logic high (+2.4V) and logic low (0 V) at the V_{MODE} pin places the PA in High Bias Mode, and a logic high

(+2.4 V) at the V_{MODE} pin places the PA in Low Bias Mode. Applying a logic low (0 V) to both the V_{EN} and V_{MODE} pins places the amplifier in shutdown (standby) mode. The Bias-mode switching of HELP™ can also be used with a DC-to-DC converter controlling the V_{CC_WCDMA} pin 21 to achieve further efficiencies at power levels under 7 dBm, though using HELP™ alone offers the best balance of improved performance, efficient use of board space, and low bill of materials cost.

EVALUATION BOARD

The evaluation board is a multilayer board using GETEK substrate, which is similar to FR4, but has a more controlled dielectric constant. The board thickness is 1.57 mm. All the routing is on the top layer (1) of a 4 layer board with a distance of 0.36 mm to the ground plane, which is on layer 2. All RF routing has been sized to present a $50\ \Omega$ impedance.

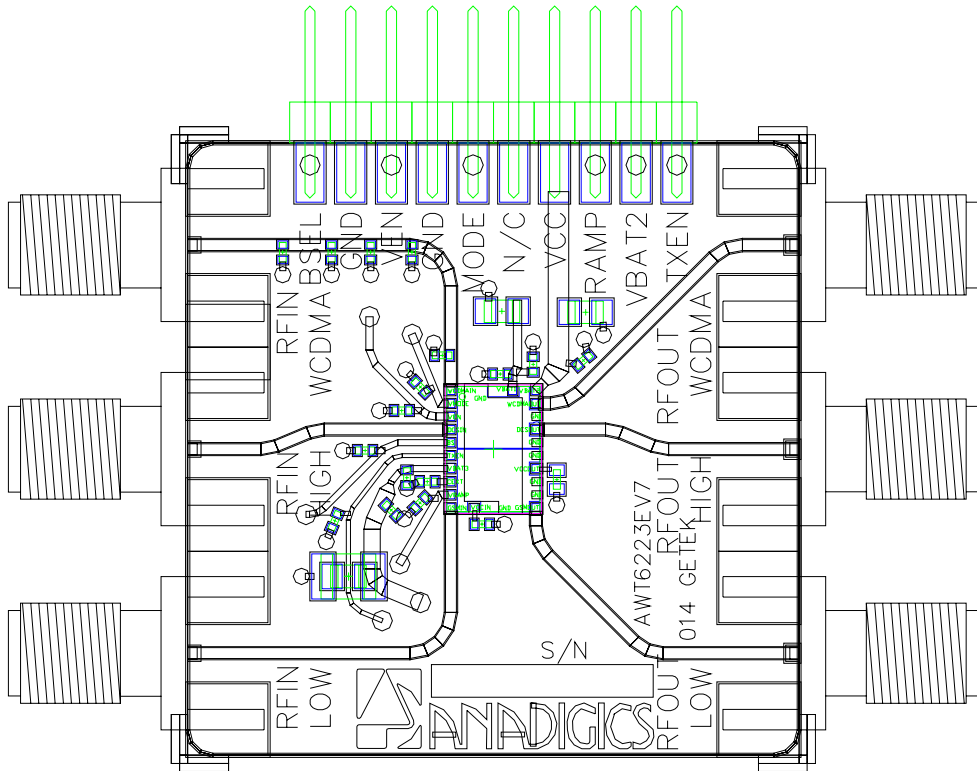


Figure 12: Evaluation Board Layout

 


Figure 13: Evaluation Board Structure

WCDMA/GSM/GPRS/Polar EDGE Power Amplifier Module


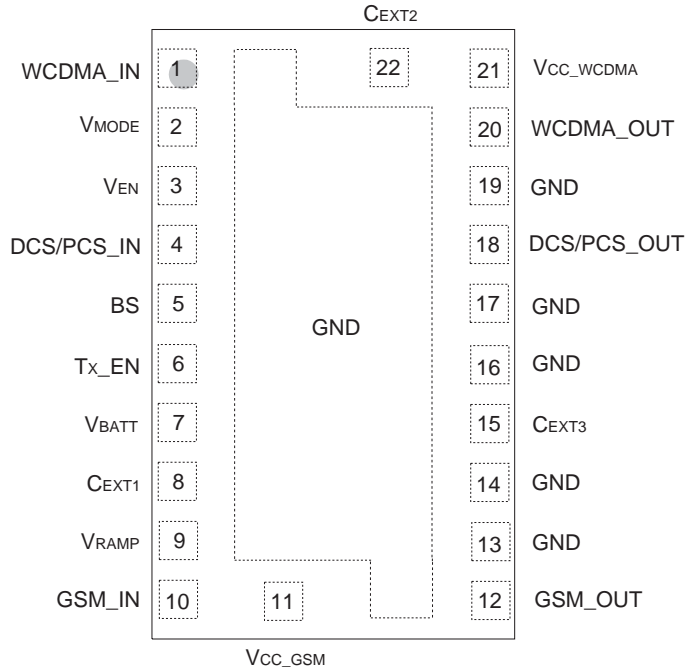


Figure 14: Pinout (X- Ray View)

Table 1: Pin Description

PIN	NAME	DESCRIPTION	PIN	NAME	DESCRIPTION
1	WCDMA_IN	WCDMA RF Input	12	GSM_OUT	GSM850/900 RF Output
2	V _{MODE}	WCDMA Mode Control Voltage	13	GND	Ground
3	V _{EN}	WCDMA Shutdown	14	GND	Ground
4	DCS/PCS_IN	DCS/PCS RF Input	15	C _{EXT3}	Bypass
5	BS	Band Select Logic Input	16	GND	Ground
6	Tx_EN	TX Enable Logic Input	17	GND	Ground
7	V _{BATT}	Battery Supply	18	DCS/PCS_OUT	DCS/PCS RF Output
8	C _{EXT1}	Bypass	19	GND	Ground
9	V _{RAMP}	Analog signal used to control the GSM output power	20	WCDMA_OUT	WCDMA RF Output
10	GSM_IN	GSM850/900 RF Input	21	V _{CC_WCDMA}	WCDMA Supply Voltage
11	V _{CC_GSM}	V _{CC} test point for GSM section. Do not connect. Do not ground.	22	C _{EXT2}	Bypass

PACKAGE OUTLINE

 

S _M B _Q L	MILLIMETERS			INCHES			NOTE
	MIN.	NOM.	MAX.	MIN.	NOM.	MAX.	
A	0.83	0.97	1.11	0.033	0.038	0.044	-
A1	-	0.31	-	-	0.012	-	-
b	0.47	-	0.53	0.019	-	0.021	20X
b1	0.54	-	0.60	0.021	-	0.023	2X
c	-	0.10	-	-	0.004	-	-
D	5.88	6.00	6.12	0.231	0.236	0.241	-
D1	3.54	-	3.66	0.139	-	0.144	-
D2	1.41	-	1.53	0.056	-	0.060	2X
E	7.88	8.00	8.12	0.310	0.315	0.320	-
E1	7.74	-	7.86	0.305	-	0.309	-
E2	6.39	-	6.51	0.252	-	0.256	-
e		0.81			0.032		-
e1		1.20			0.047		2X
L	0.47	-	0.53	0.019	-	0.021	-

NOTES:

1. CONTROLLING DIMENSIONS: MILLIMETERS
2. UNLESS SPECIFIED TOLERANCE=±0.076[0.003].
3. PADS (INCLUDING CENTER) SHOWN UNIFORM SIZE FOR REFERENCE ONLY. ACTUAL PAD SIZE AND LOCATION WILL VARY WITHIN MIN. AND MAX. DIMENSIONS ACCORDING TO SPECIFIC LAMINATE DESIGN.

Figure 16: Package Outline - 22 Pin 6 mm x 8 mm x 1 mm Surface Mount Package

 


Figure 17: Recommended PCB Metal

 


Figure 18: Recommended PCB Solder Mask

NOTES

NOTES



ANADIGICS, Inc.

141 Mount Bethel Road
Warren, New Jersey 07059, U.S.A.
Tel: +1 (908) 668-5000
Fax: +1 (908) 668-5132

URL: <http://www.anadigics.com>
E-mail: Mktg@anadigics.com

IMPORTANT NOTICE

ANADIGICS, Inc. reserves the right to make changes to its products or to discontinue any product at any time without notice. The product specifications contained in Advanced Product Information sheets and Preliminary Data Sheets are subject to change prior to a product's formal introduction. Information in Data Sheets have been carefully checked and are assumed to be reliable; however, ANADIGICS assumes no responsibilities for inaccuracies. ANADIGICS strongly urges customers to verify that the information they are using is current before placing orders.

WARNING

ANADIGICS products are not intended for use in life support appliances, devices or systems. Use of an ANADIGICS product in any such application without written consent is prohibited.